

EE4226 - EXPERIMENT #1

LABORATORY PRACTICES, BASIC MEASUREMENTS, AND SAFETY

Lab Section: L02

Name: Jacob Cox

Date: 1/24/2018

Lab Partners: MITch Marford

Sean James

Part 1: (Checkmark the meters you have)

2. Dual DC Voltmeter	<u>X</u>	Dual DC Ammeter	<u>X</u>
DC Volt/Ammeter	<u>X</u>		
Dual AC Voltmeter	<u>X</u>	AC Ammeter with CT	<u>X</u>
AC Volt/Ammeter	<u>X</u>	AC Wattmeter	<u>X</u>
Fluke 289 Multimeter	<u>X</u>		

Part 2:

7. $V_{dc} = \underline{90}$ Volts $I_{dc} = \underline{2.3}$ Amps $I_{Clamp} = \underline{\quad}$ Amps $P_{dc} = \underline{207}$ Watts

8. $V_{dc} = \underline{90}$ Volts, $I_{dc} = \underline{8.1}$ Amps, $I_{Clamp} = \underline{\quad}$ Amps $P_{dc} = \underline{729}$ Watts

Part 3:

12. $V = \underline{120}$ Volts $I = \underline{3.4}$ Amps $I_{Clamp} = \underline{3.5}$ Amps $P = \underline{46}$ Watts
p.f. = (Inductive - LOAD)

13. $V = \underline{120}$ Volts $I = \underline{5.8}$ Amps $I_{Clamp} = \underline{5.8}$ Amps $P = \underline{563}$ Watts
p.f. = (Resistive - Inductive - LOAD)

14. $V = \underline{120}$ Volts $I = \underline{4.8}$ Amps $I_{Clamp} = \underline{4.8}$ Amps $P = \underline{560}$ Watts
p.f. = (Resistive - Inductive - Capacitive - LOAD)

2x30μF

3x150W