

EE4226 - EXPERIMENT #3

IDEAL SINGLE PHASE TRANSFORMERS

Lab Section: LO2

Name: Jacob Cohen

Date: 2/14/2018

Lab Partners: Mitch Marford

Part 1:

3. Resistance  $H_1 - H_3$  1.588

Resistance  $X_1 - X_2$  0.451

High Voltage Coil H

Low Voltage Coil V

Part 2:


5. Voltage  $H_1 - H_3$  119.3

Voltage  $X_1 - H_3$  188.12

7. Voltage  $H_1 - H_3$  120.26

Voltage  $X_2 - H_3$  50.84

8. Draw the polarity marks

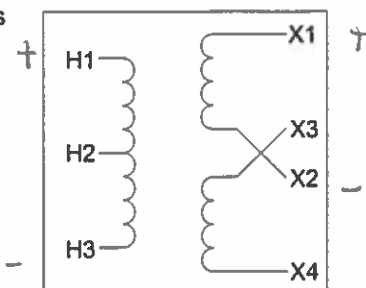

Part 3:

10. Voltage  $H_1 - H_3$  208.2

Voltage  $X_1 - X_4$  239.8

11. Voltage  $H_1 - H_3$  208.4

Voltage  $X_1 - X_3$  0.1525

Part 4:

14.  $V_{in}$  150.1

$I_{in}$  1.0A

$R_{measured}$  49.98

$V_{out}$  85.77

$I_{out}$  1.7A

$R_{calculated}$  \_\_\_\_\_

$I_{coil1}$  1.0

$I_{coil2}$  0.8A


Part 5:

18. Voltage  $H_1 - X_2$  197.9  
 Voltage  $X_1 - X_2$  68.65  
 Current  $H_1 - H_3$  3.8A

Voltage  $H_1 - H_3$  127.8  
 Load Current 4.25  
 Current  $X_1 - X_2$  6.1A

Part 6:

20. Sketch your circuit below:

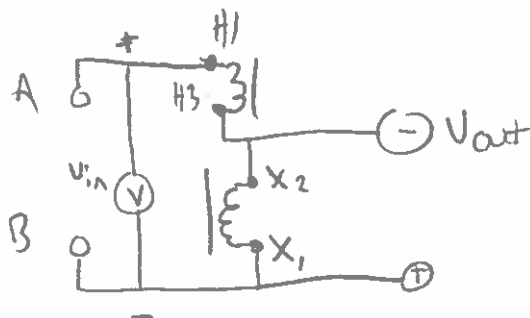

Voltage  $H_1 - H_3$  207  
 $V_{IN}$  88.3

Voltage  $X_1 - X_2$  119.21  
 $V_{OUT}$  119.21